

Fall 2016 – CS2420

Homework 7

Due Date : Wednesday - November 30th , 2016 class time

- 1) Using The Moore Model , create a state diagram for the following candy machine .
 - The machine Release item after 25 cents are deposited
 - The machine has a Single coin slot for quarters , dimes, nickels
 - The machine will not return any changes back.
- 2) Design a four-bit priority encoder with the following input but with the priority of input $D_2 > D_1 > D_0 > D_3$

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

- Construct the Truth Table
- Use K-map to get the simplest function for each output
- Implement the circuit

3) A combinational circuit is specified by the following Boolean function :

$$F_1 (A , B , C) = \sum_m (2 , 5 , 6)$$

$$F_2 (A , B , C) = \sum_m (1 , 3 , 4)$$

- Implement the circuit with a 3 x 8 decoder and OR gates. Use block diagram for the decoder

4) Implement the following Boolean function with a 4 x 1 multiplexer.

$$F (A , B , C) = \sum (1 , 2 , 5 , 7)$$

Note : Each Question worth 25 points.

Remarks :

- The homework does not have to be typed , however , it must be written using **pencils** only . Include the following information on **the top left** hand side of the first page :-
 - Your Name :
 - Your Roster or Serial Number :
 - Homework Number : 7
 - Due Date : November 30th , 2016
- **Make sure that you write the question first then followed by your answer.**
- The homework must also be uploaded using homework upload no later than the end of class time on the due date. Use the following name format for your file name
**LastName_FirstName_CS2420-A7.zip or
LastName_FirstName_CS2420-A7.pdf or
LastName_FirstName_CS2420-A7.doc**
- For each question , you must **show** all your work.
- **Missing ANY of the above items from your assignment will result in deducting 15 % of the assignment grade. NO EXCEPTIONS.**

Turn in hard copy of your assignment no later no than the end of class time on the due date. The hard copy must be **stapled**. **No Late assignment will be accepted and a grade of zero will be assigned.** If you are absent on the assignment's due date , a grade of zero will be recorded .

- **Copying the assignment from others will result in grade ZERO.**