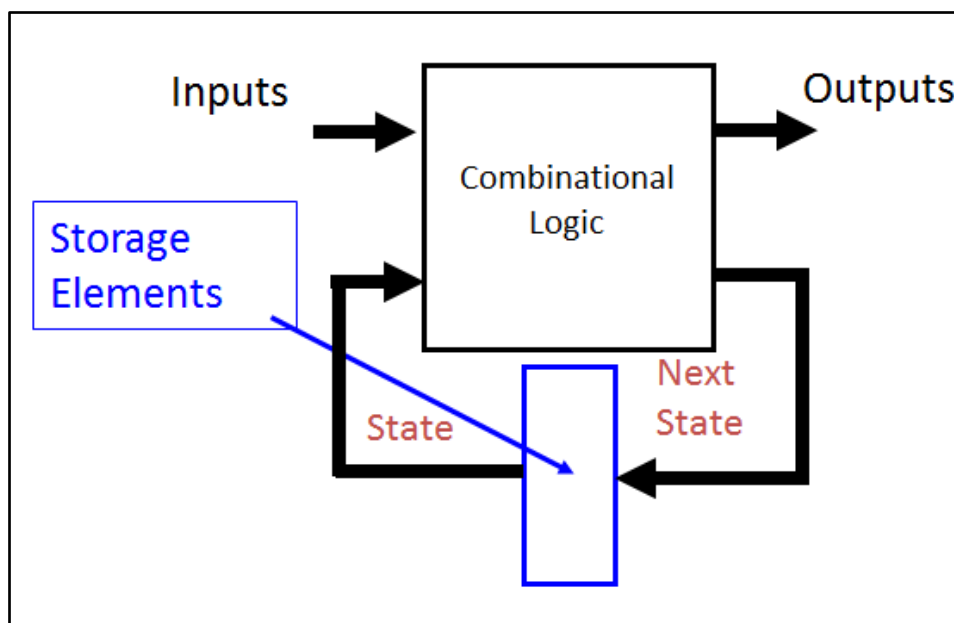


Outline


- Introduction to sequential circuits
- Types of sequential circuits
- Storage elements
 - ***Flip-flops***

Introduction to Sequential Circuits

- A Sequential circuit contains:
 - Storage elements:
Latches or Flip-Flops
 - Combinational Logic:
 - **Implements a multiple-output switching function**
 - Signals from the outside are **inputs**.
 - Signals to the outside are **outputs**.
 - **Other inputs**, State or Present State, are signals from storage elements.
 - **The remaining outputs**, Next State are **inputs to storage elements**.



- Combinatorial Logic

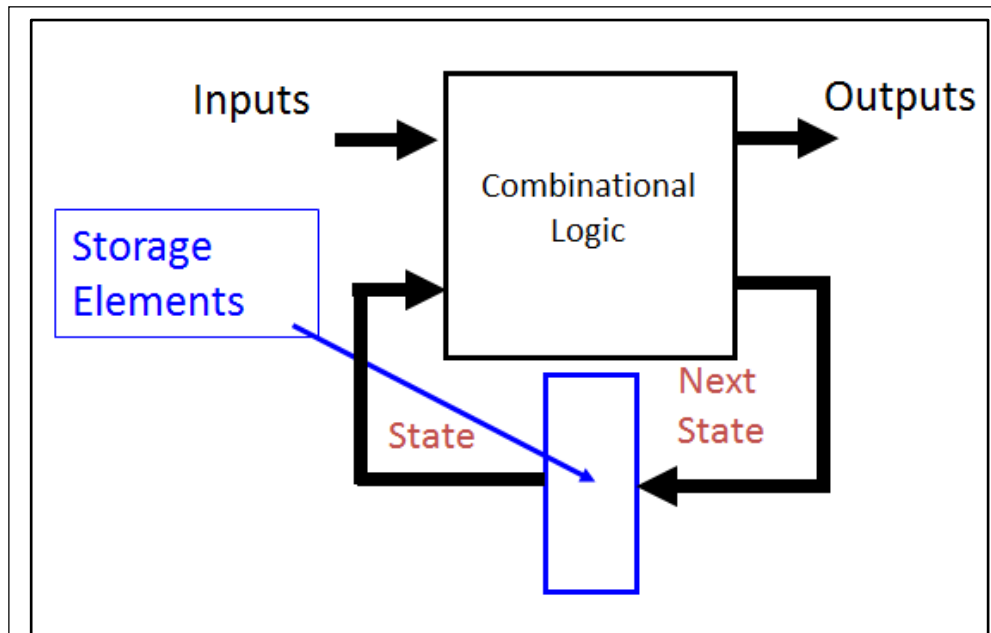

- Next state function*
 $\text{Next State} = f(\text{Inputs}, \text{State})$
- Output is a function of inputs and State.*

Types of Sequential Circuits

- Depends on the times at which:
 - storage elements observe their inputs, and
 - storage elements change their state
- Synchronous
 - Behavior defined from knowledge of its signals at discrete instances of time
 - Storage elements observe inputs and can change state only in relation to a timing signal (clock pulses from a clock)
- Asynchronous
 - Behavior
 - r defined from knowledge of inputs an any instant of time and the order in continuous time in which inputs change
 - Nevertheless, the synchronous abstraction makes complex designs tractable!


Storage element

- **Storage elements:** devices capable of storing binary information

flip-flop: used in clocked sequential circuit, storing one bit of information: state

The flip-flop is updated when a pulse of the clock signal occurs.


Latch: basic component of flip-flop.

 


Basic (NAND) S – R ([Set-Reset latch](#)) Latch

- “Cross-Coupling” two NAND gates gives the S' -R' (Set – Reset) Latch:

Which has the time sequence behavior:

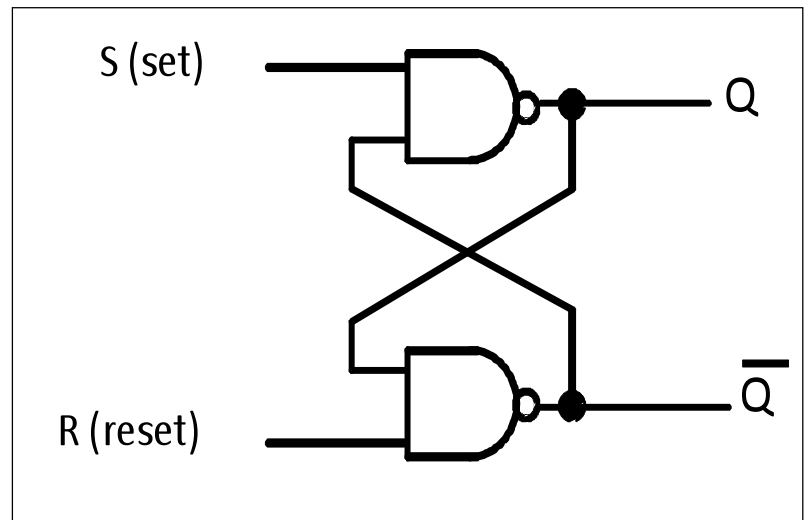


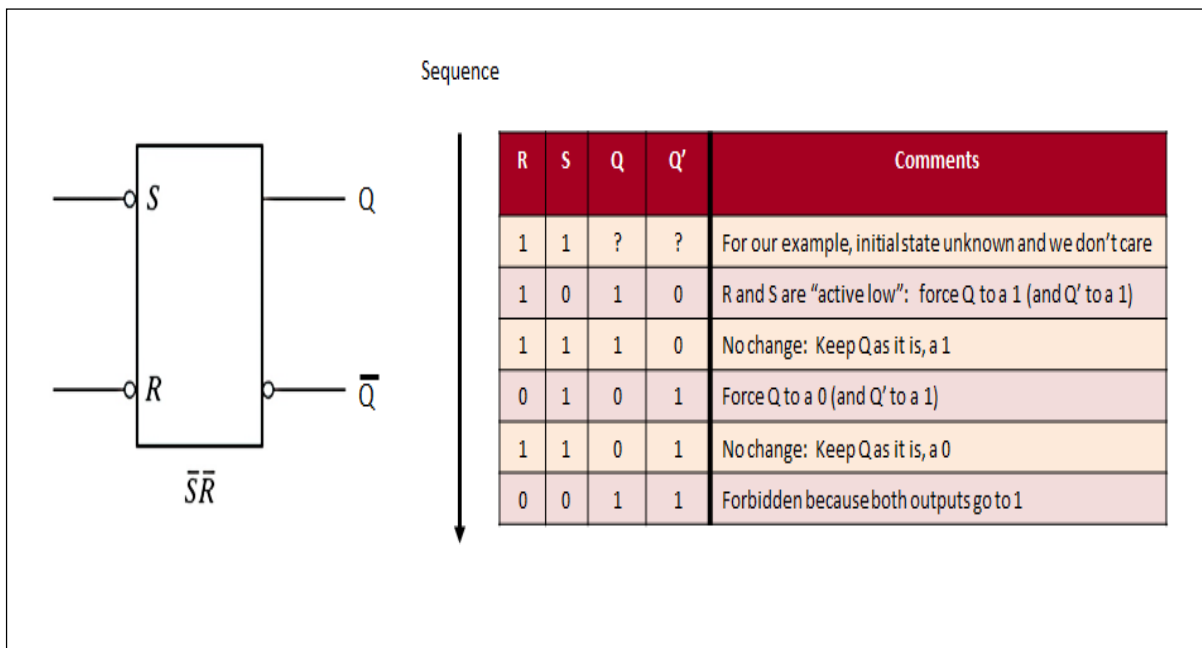$S = 0, R = 0$ is forbidden as input pattern



D Latch

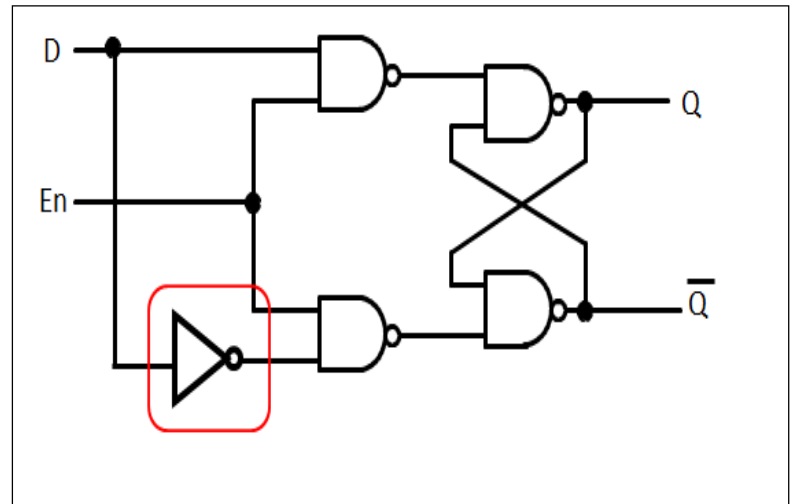
- Adding an inverter to the S-R Latch, gives the D Latch



(shown with an enable input)

The enable input often acts as the clock.

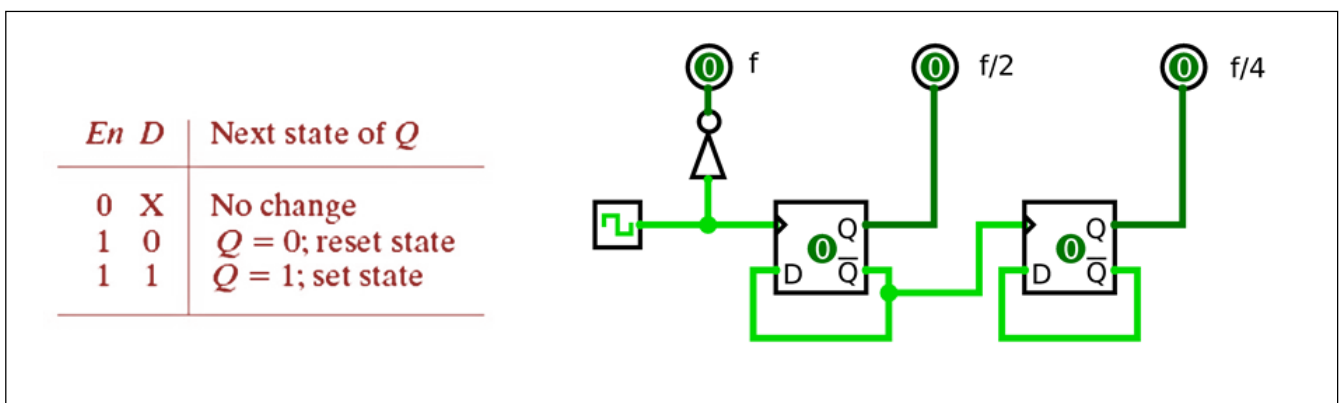- Note that there are no “indeterminate” states!



Flip-Flops

- The latch timing problem
- Edge-triggered flip-flop
- Direct inputs to flip-flops



The Latch Timing Problem

- In a sequential circuit, paths may exist through combinational logic:
 - From one storage element to another
 - From a storage element back to the same storage Element
- The combinational logic between a latch output and a latch input may be as simple as an interconnect
- For a D-latch, the output Q depends on the input D whenever the control input En has value 1

The Latch Timing Problem

- Consider the following circuit:
- Suppose that initially $Y = 0$.


<i>En</i>	<i>D</i>	Next state of <i>Q</i>
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

  

- As long as $En = 1$, the value of Y continues to change!
- The changes are based on the delay present on the loop through the connection from Y back to Y .
- This behavior is clearly unacceptable.
- Desired behavior: Y changes only once per clock pulse


Flip-Flop Solution

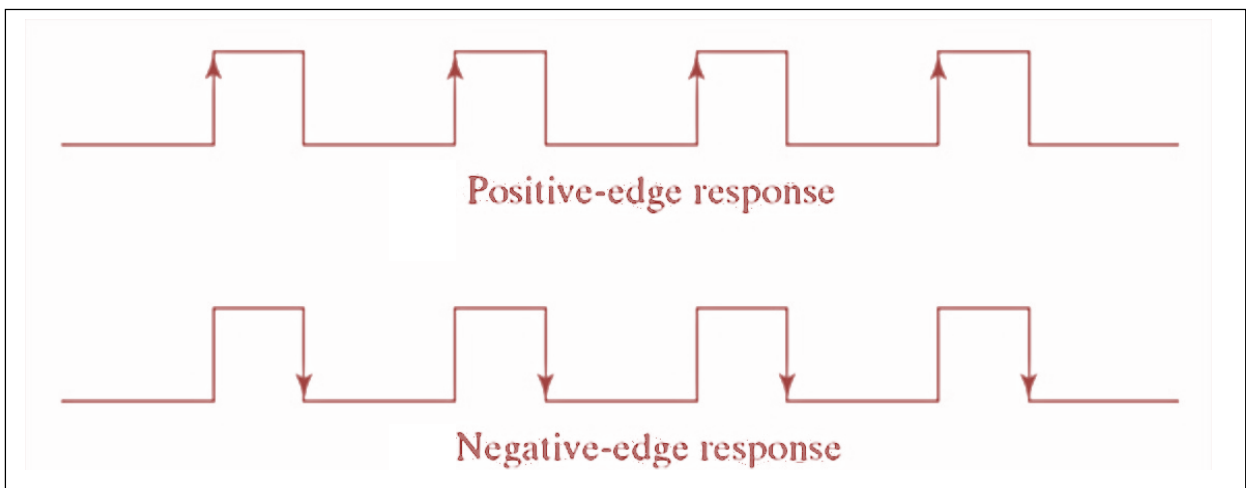- An *edge-triggered* flip-flop ignores the pulse while it is at a constant level and triggers only during a transition of the clock signal
- Edge-triggered flip-flops can be built directly at the electronic circuit level




Edge-Triggered D Flip-Flop

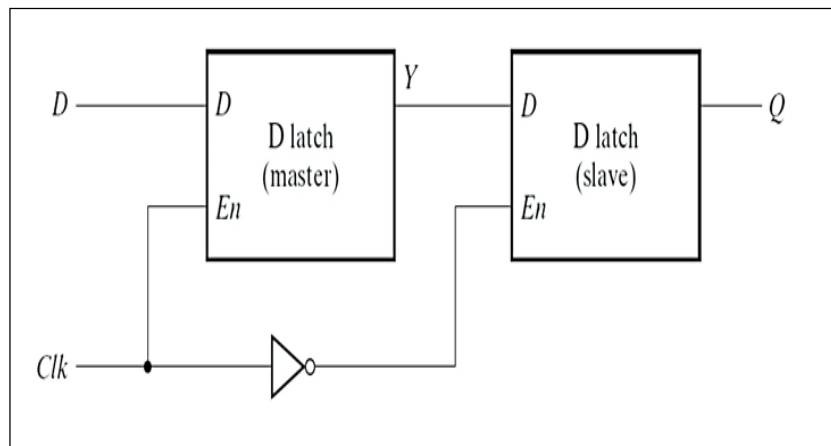- The edge-triggered D flip-flop is the master-slave D flip-flop



 
- The change of the D flip-flop output is associated with the negative edge at the end of the pulse




- It is called a ***negative-edge triggered*** flip-flop

Positive-Edge Triggered D Flip-Flop

 
- Formed by adding inverter to clock input



 - Q changes to the value on D applied at the positive clock edge within timing constraints to be specified




- Our choice as the standard circuits

 

quential

Direct Inputs

 - At power up or at reset, all or part of a sequential circuit usually is initialized to a known state before it begins operation
- This initialization is often done outside of the clocked behavior of the circuit, i.e., asynchronously.



- Direct R inputs that control the state of the latches within the flip-flops are used for this initialization.
- For the example flip-flop shown
 - 0 applied to R resets the flip-flop to the 0 state

R	Clk	D	Q	Q'
0	X	X	0	1
1	\uparrow	0	0	1
1	\uparrow	1	1	0

(b) Function table